
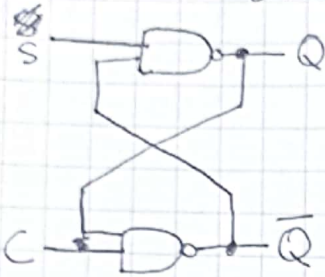


- NAND Gate Latch

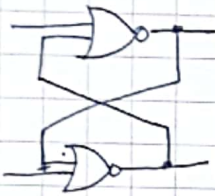


S	C	Q_{n+1}	\bar{Q}_{n+1}	Remarks
0	0	1	1	No change
0	1	1	0	Set (0)
1	0	0	1	Clear (1)
1	1	Q_n	\bar{Q}_n	No change

- NOR Gate Latch




S	C	Q_{n+1}	\bar{Q}_{n+1}	Remarks
0	0	Q_n	\bar{Q}_n	No change
0	1	0	1	clear (0)
1	0	1	0	set (1)
1	1	0	0	Invalid


- Clocked SC Flip Flop

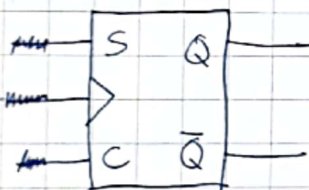

S	C	CLK	Q
0	0	↑	No change
0	1	↑	0
1	0	↑	1
1	1	↑	Invalid

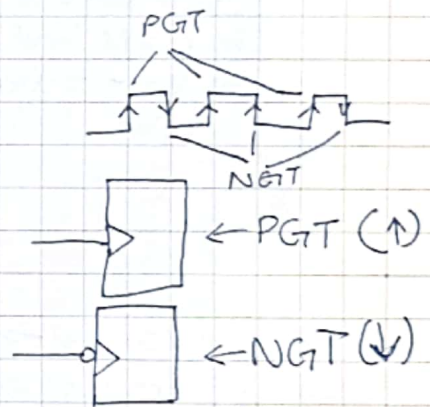


- Clocked JK Flip Flop

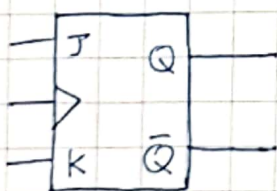

S	C	CLK	Q
0	0	↑	Q_n , No change
0	1	↑	0
1	0	↑	1
1	1	↑	\bar{Q}_n , Toggle

- Data Flip Flop (PGT)

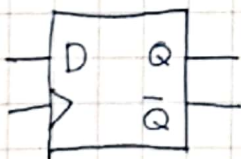

D	CLK	Q
0	↑	0
1	↑	1

Output follows Input.


- Data Flip Flop (NGT)



D	CLK	Q
0	↓	0
1	↓	1

Q follows D at clock

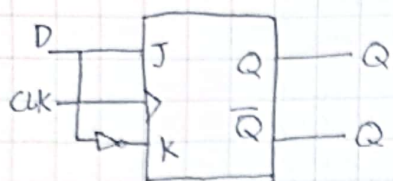- Data Flip Flops ~~can~~ using JK Flip Flop.



D	K	CLK	Q
0	0	↑	No change change
0	1	↑	0
1	0	↑	1
1	1	↑	\bar{Q}_0

- D Latch



* No triangle at the ~~EN~~ EN input
→ level-triggered input.


EN	D	Q
0	X	No change change
1	0	0
1	1	1

→ Q only follows D when EN is active (1).

→ Synchronous → ~~CLK~~ CLK.

→ Asynchronous → Preset & clear

↳ Preset → make the output to 1.

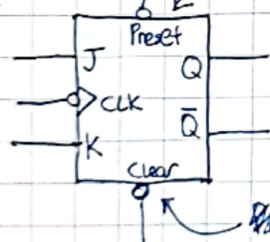


~~Reset~~ Clear → make the output to 0.

Monostable \rightarrow 1 stable state \rightarrow one shot.

Bistable \rightarrow 2 stable state \rightarrow Flip Flip / multivibrator.

Astable \rightarrow No stable state \rightarrow constantly changing \rightarrow oscillator

One shot.

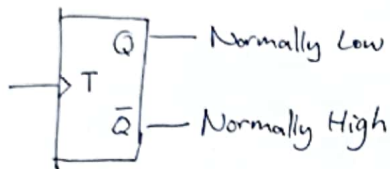

Schmitt - Trigger oscillator generates rectangular pulse
FF can change the frequency of rectangular pulse
One shot can change the pulse width of rectangular pulse

It has a stable output state, normally $Q = 0$

When T is triggered, it switches to Quasi-stable state ($Q = 1$) for a fixed period, t_p .


Non-retriggerable one-shot don't respond to trigger during Quasi stable state.

Retriggerable ~~can~~ can be retriggered while it is in the Quasi stable state.


Schmitt - Trigger Inverter.

\rightarrow 7404.

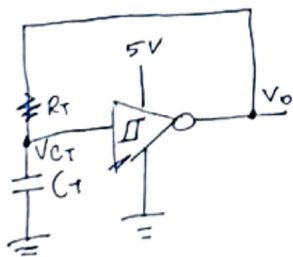Oscillations may occur at output if input stays in the forbidden region (neither "0" nor "1") for too long.



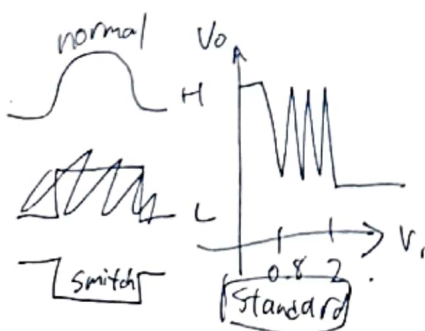Assume V_O was H initially. C_T will charge towards V_O , when V_{CT} goes above V_{T+} , V_O switch to L. This cause C_T to discharge, when V_{CT} goes below V_{T-} , V_O switch to H. This causing C_T to charge up again. This cycle repeats results in rectangular pulse at V_O .



increasing input must go higher than V_{T+} for the out to go L.
decreasing input must go lower than V_{T-} for the output to switch to H.